

TEIS**Technical report**

Author Jasim Abbasi		Task		
Email engr.jasim@gmail.com	Approved		Version	File VHDL-4

TEIS

Assignment 4 VHDL Course

Designing the door lock system

Jasim Abbasi**2014-10-04**

The basic purpose of this project is to design the two different types of automatic door lock system. A simple door and a door with more advance door lock system.

CONTENTS

CONTENTS	1
1 INTRODUCTION	2
1.1 Background	2
2 REQUIREMENTS SPECIFICATION	2
2.1 System requirements.....	2
2.2 Functional requirements	2
2.3 Construction code requirements	2
2.4 Delivery requirements.....	2
3 TEST PROTOCOL	2
4 VERIFICATION	4
4.1 Result from simulation	4
Simple door moore machine.....	4
Simple door mealy machine	5
Advance door	5
Simple door moore VHDL Code	6
Simple door moore Do file	7
Simple door test bench.....	8
Simple door mealy VHDL Code	12
Simple door mealy do file.....	14
Synchronous mealy VHDL Code.....	15
Synchronous do file.....	16
Advance door VHDL	18
Advance door mealy do file.....	21
Advance door Test bench	22

1 INTRODUCTION

1.1 Background

A new customer has ordered prototypes of an automatic door control structure to be made in two different versions,

- Småland customers want a simpler (cheaper) than those living Stockholm.
- A simple door and a more advanced door with lock.

2 REQUIREMENTS SPECIFICATION

2.1 System requirements

The system requirement from the customer is that the design should be made with two different types of state machines and want it single door controller with both synchronous outputs (Mealy + Moore).

2.2 Functional requirements

The client has a requirement to design two different types of door lock system.

- Simple door lock system
- Advance door lock system

2.3 Construction code requirements

The client has requirements that code should be written in VHDL and result should be simulate on the modelsim.

2.4 Delivery requirements

The delivery of the product should be before 6 October, 2014.

3 TEST PROTOCOL

The table 1 and 2 shown the functionality of simple and advance door lock system.

KEY1	KEY0	LEDG1	LEDG0	Description
0	1	1	0	When door is closed
1	0	0	1	When door is open

Table 1: Simple door test protocol

 


Figure 1: Simple door Stateflow diagram

KEY3	KEY2	KEY1	KEY0	LEDG2	LEDG1	LEDG0	LEDR1	Description
0	0	0	1	0	1	0	0	Door is close
0	0	1	0	0	0	1	0	Door is open
0	1	0	0	1	0	0	0	Door is lock
1	0	0	0	0	0	0	1	Error

Table 2: Advance door test protocol

 


Figure 2: Advance door Stateflow diagram

4 VERIFICATION

4.1 Result from simulation

The tables 3 and 4 shows the test protocol of verifying simple and advance doors. The results can be verified on modelsim.


Case no	Description	OK	Verifying (Modelsim)	Validation (DE2-115)
1	Reset=0	LEDG=01 (door open)	OK	OK
2	Key=10	LEDG=10 (door close)	OK	OK
3	Key=01	LEDG=01 (door open)	OK	OK
4	Key=10	LEDG=10 (door close)	OK	OK
5	Reset=0	LEDG=01 (door open)	OK	OK

Table 3: Test protocol of verifying simple door


Case no	Description	OK	Verifying (Modelsim)	Validation (DE2-115)
1	Reset=0 Door open	LEDG=001 LEDR=0	OK	OK
2	Key=0001 Close	LEDG=010 LEDR=0	OK	OK
3	Key=0100 Lock	LEDG=100 LEDR=0	OK	OK
4	Key=1000 Error	LEDG=000 LEDR=1	OK	OK
5	Key=1111 Error	LEDG=000 LEDR=1	OK	OK

Table 4: Test protocol of verifying advance door


Simple door moore machine

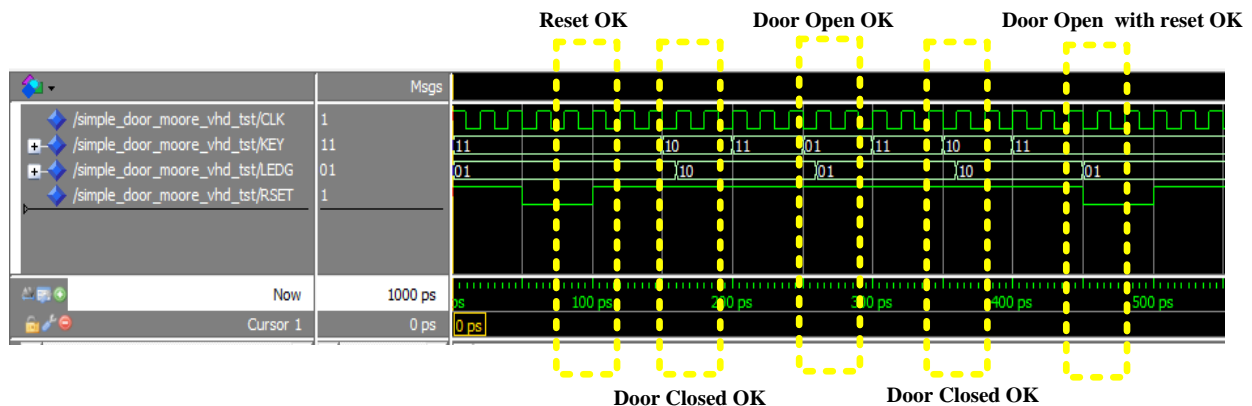


Simple door mealy machine

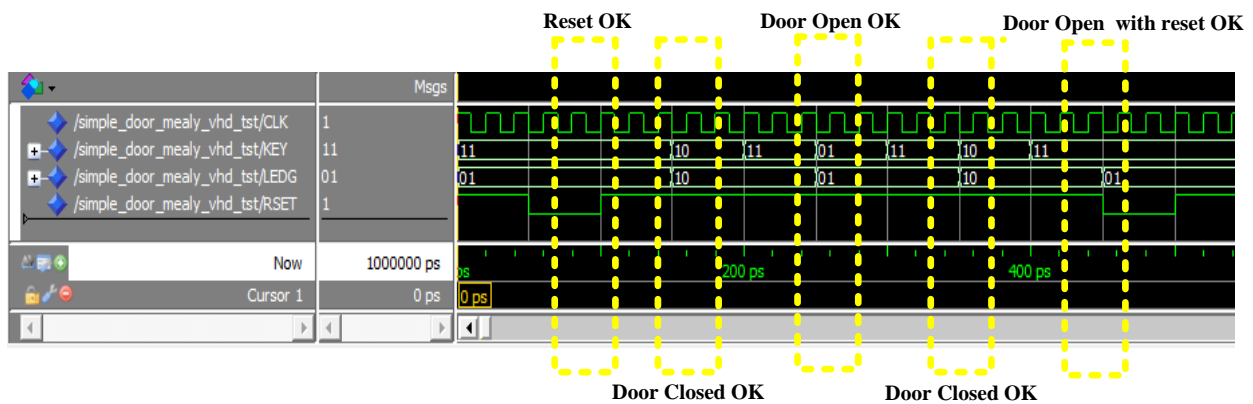

Simple door synchronous outputs

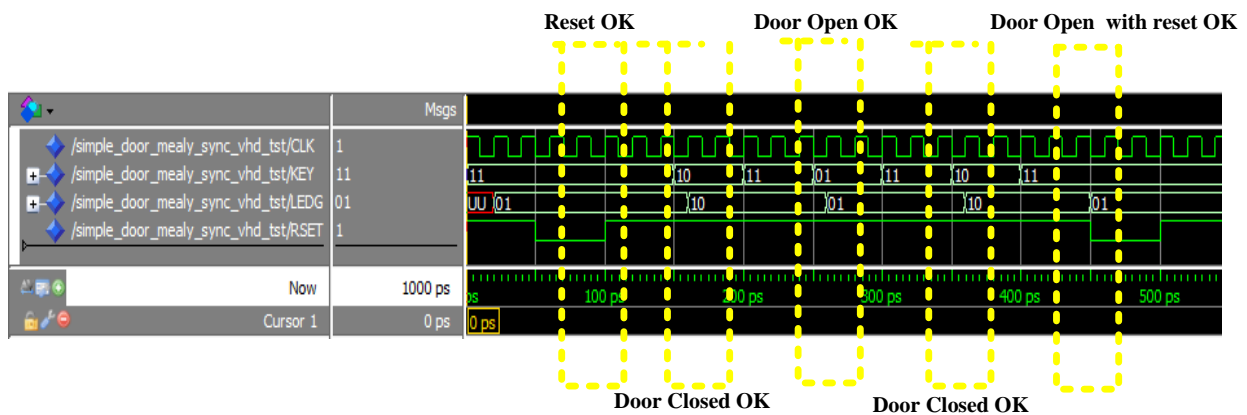

Advance door

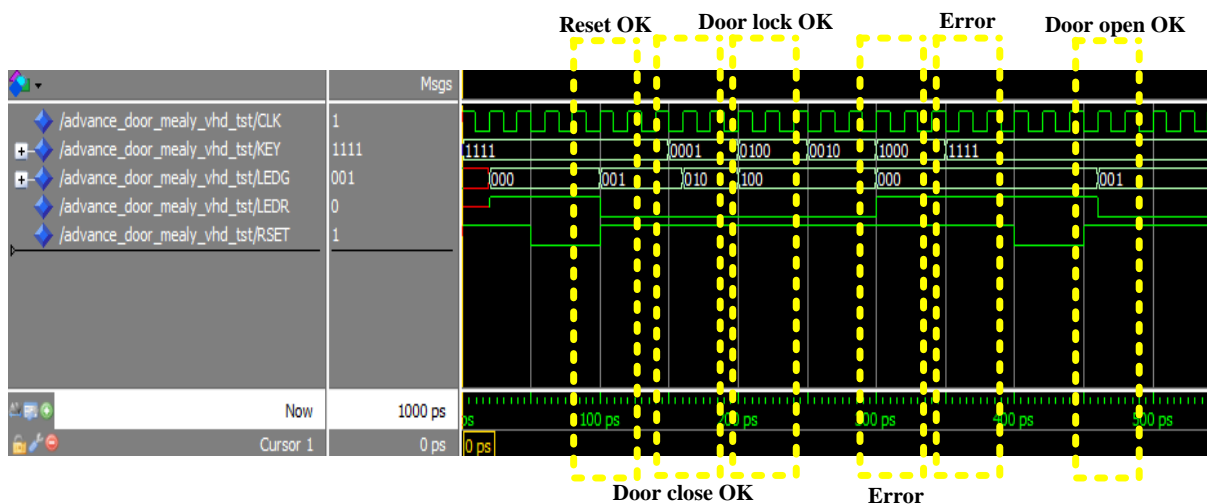

APPENDIX

Simple door moore VHDL Code

```
LIBRARY ieee;

use ieee.std_logic_1164.all;

use ieee.std_logic_arith.all;

use ieee.std_logic_unsigned.all;

entity simple_door_moore is
    port
    (
        CLK: in std_logic; -- Active on positiv flank
        RSET: in std_logic;
        KEY: in std_logic_vector(1 downto 0); -- address in slide switches
        LEDG: out std_logic_vector(1 downto 0) -- data in slide switches
    );
end entity;

architecture model of simple_door_moore is
    type STATE_TYPE is (oppen, close);
    signal state: STATE_TYPE;
begin
    clk_reset: PROCESS (rset, clk)
    BEGIN
        IF (rset='0') THEN
            state<= oppen;
        ELSIF rising_edge(clk) THEN
            case state is
                when oppen =>
```

```

        if(KEY = "10") then
            state<= close;
        end if;

        when close =>
            if KEY = "01" then
                state<= oppen;
            end if;

            when others=>
                state<= oppen;

        end case ;

    end if;

--end if;

end process;

process(state)
begin
    case state is
        when oppen=>
            LEDG<="01";
        when close=>
            LEDG<="10";
        end case;
    end process;

end model;

```

Simple door moore Do file

onerror {resume}

quietly WaveActivateNextPane {} 0


```

add wave -noupdate /simple_door_moore_vhd_tst/CLK
add wave -noupdate /simple_door_moore_vhd_tst/KEY
add wave -noupdate /simple_door_moore_vhd_tst/LEDG
add wave -noupdate /simple_door_moore_vhd_tst/RSET
TreeUpdate [SetDefaultTree]
WaveRestoreCursors {{Cursor 1} {0 ps} 0}
quietly wave cursor active 0
configure wave -namecolwidth 224
configure wave -valuecolwidth 100
configure wave -justifyvalue left
configure wave -signalnamewidth 0
configure wave -snapdistance 10
configure wave -datasetprefix 0
configure wave -rowmargin 4
configure wave -childrowmargin 2
configure wave -gridoffset 0
configure wave -gridperiod 1
configure wave -griddelta 40
configure wave -timeline 0
configure wave -timelineunits ps
update
WaveRestoreZoom {0 ps} {931 ps}

```

Simple door test bench

```

LIBRARY ieee;

USE ieee.std_logic_1164.all;

```

```

ENTITY simple_door_moore_vhd_tst IS

END simple_door_moore_vhd_tst;

ARCHITECTURE simple_door_moore_arch OF simple_door_moore_vhd_tst IS

-- constants

-- signals

SIGNAL CLK : STD_LOGIC;

SIGNAL KEY : STD_LOGIC_VECTOR(1 DOWNTO 0);

SIGNAL LEDG : STD_LOGIC_VECTOR(1 DOWNTO 0);

SIGNAL RSET : STD_LOGIC;

COMPONENT simple_door_moore

    PORT (

        CLK : IN STD_LOGIC;

        KEY : IN STD_LOGIC_VECTOR(1 DOWNTO 0);

        LEDG : OUT STD_LOGIC_VECTOR(1 DOWNTO 0);

        RSET : IN STD_LOGIC

    );

END COMPONENT;

BEGIN

    i1 : simple_door_moore

    PORT MAP (

-- list connections between master ports and signals

        CLK => CLK,

        KEY => KEY,

        LEDG => LEDG,

        RSET => RSET

```

```

    );
clk_signal: process
begin
    -----CLOCK SIGNAL-----

    clk<='1';

        wait for 10 ps;

        --wait on clk;

    clk<='0';

    wait for 10 ps;

        --wait on clk;

end process;

init : PROCESS
-- variable declarations

BEGIN

    -- code that executes only once

    KEY<= "11"; --

        rset<='1';

        wait for 50ps ;

        rset<='0';

        wait for 50ps ;

        rset<='1';

    -----CASE 2-----

        wait for 50ps ;

    KEY<= "10"; --

        wait for 50ps ;

        KEY<= "11";

```

```

-----CASE 2-----
    wait for 50ps ;
KEY<= "01"; --
    wait for 50ps ;
    KEY<= "11";
-----CASE 3-----
    wait for 50ps ;
KEY<= "10"; --
    wait for 50ps ;
    KEY<= "11";
-----CASE 4-----
    wait for 50ps ;
    rset<='0';
    wait for 50ps ;
    rset<='1';

-- -----
-- KEY<= "00"; --
-- wait for 50ps ;
WAIT;
END PROCESS init;
always : PROCESS
-- optional sensitivity list
-- (    )
-- variable declarations
BEGIN
    -- code executes for every event on sensitivity list

```

```
WAIT;
```

```
END PROCESS always;
```

```
END simple_door_moore_arch;
```

Simple door mealy VHDL Code

```
LIBRARY ieee;
```

```
use ieee.std_logic_1164.all;
```

```
use ieee.std_logic_arith.all;
```

```
use ieee.std_logic_unsigned.all;
```

```
entity simple_door_mealy is
```

```
    port
```

```
    (
```

```
        CLK: in std_logic; -- Clock signal
```

```
        RSET: in std_logic; --reset signal
```

```
        KEY: in std_logic_vector(1 downto 0); -- Input keys
```

```
        LEDG: out std_logic_vector(1 downto 0) -- output key
```

```
    );
```

```
end entity;
```

```
    architecture model of simple_door_mealy is
```

```
        type STATE_TYPE is (open, close);
```

```
        signal current_state,next_state: STATE_TYPE;
```

```
        signal state: STATE_TYPE;
```

```
    begin
```

```
        clk_reset: PROCESS (rset,clk)
```

```
        BEGIN
```

```
            IF (rset='0') THEN
```

```
                state<= open;
```

```

ELSIF rising_edge(clk) THEN
    case state is
        when oppen =>
            if(KEY = "10") then
                state<= close;
            end if;
            when close =>
                if KEY = "01" then
                    state<= oppen;
                end if;
                when others=>
                    state<= oppen;
            end case ;
        end if;
    --end if;
end process;
process(state,key)
begin
    case state is
        when oppen=>
            if(KEY = "01" or KEY = "11")then
                LEDG<="01";
            else
                LEDG<="10";
            end if;
        when close=>

```

```

        if(KEY = "10" or KEY = "11") then
            LEDG<="10";
        else
            LEDG<="01";
        end if;
    end case;
end process;
end model;

```

Simple door mealy do file

```

onerror {resume}

quietly WaveActivateNextPane {} 0

add wave -noupdate /simple_door_mealy_vhd_tst/CLK
add wave -noupdate /simple_door_mealy_vhd_tst/KEY
add wave -noupdate /simple_door_mealy_vhd_tst/LEDG
add wave -noupdate /simple_door_mealy_vhd_tst/RSET

TreeUpdate [SetDefaultTree]

WaveRestoreCursors {{Cursor 1} {0 ps} 0}

quietly wave cursor active 0

configure wave -namecolwidth 220
configure wave -valuecolwidth 100
configure wave -justifyvalue left
configure wave -signalnamewidth 0
configure wave -snapdistance 10
configure wave -datasetprefix 0
configure wave -rowmargin 4
configure wave -childrowmargin 2

```

```
configure wave -gridoffset 0
configure wave -gridperiod 1
configure wave -griddelta 40
configure wave -timeline 0
configure wave -timelineunits ps
update
WaveRestoreZoom {0 ps} {935 ps}
```

Synchronous mealy VHDL Code

```
LIBRARY ieee;

use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity simple_door_mealy_sync is
    port
    (
        CLK: in std_logic; -- Clock signal
        RSET: in std_logic; -- reset signal
        KEY: in std_logic_vector(1 downto 0); -- Input keys
        LEDG: out std_logic_vector(1 downto 0) -- outputs
    );
end entity;

architecture model of simple_door_mealy_sync is
    type STATE_TYPE is (open, close);
    signal current_state,next_state: STATE_TYPE;
    signal state: STATE_TYPE;
begin
```



```

clk_reset: PROCESS (rset,clk)
BEGIN
    IF (rset='0') THEN
        state<= oppen;
        LEDG<="01";
    ELSIF rising_edge(clk) THEN
        case state is
            when oppen =>
                LEDG<="01";
                if(KEY = "10") then
                    LEDG<="10";
                    state<= close;
                end if;
                when close =>
                    LEDG<="10";
                    if KEY = "01" then
                        LEDG<="01";
                        state<= oppen;
                    end if;
                end case ;
            end if;
        --end if;
    end process;
end model;

```

Synchronous do file

```
onerror {resume}
```

```
quietly WaveActivateNextPane {} 0
add wave -noupdate /simple_door_mealy_sync_vhd_tst/CLK
add wave -noupdate /simple_door_mealy_sync_vhd_tst/KEY
add wave -noupdate /simple_door_mealy_sync_vhd_tst/LEDG
add wave -noupdate /simple_door_mealy_sync_vhd_tst/RSET
TreeUpdate [SetDefaultTree]
WaveRestoreCursors {{Cursor 1} {0 ps} 0}
quietly wave cursor active 0
configure wave -namecolwidth 239
configure wave -valuecolwidth 100
configure wave -justifyvalue left
configure wave -signalnamewidth 0
configure wave -snapdistance 10
configure wave -datasetprefix 0
configure wave -rowmargin 4
configure wave -childrowmargin 2
configure wave -gridoffset 0
configure wave -gridperiod 1
configure wave -griddelta 40
configure wave -timeline 0
configure wave -timelineunits ps
update
WaveRestoreZoom {0 ps} {917 ps}
```

Advance door VHDL

```
LIBRARY ieee;

use ieee.std_logic_1164.all;

use ieee.std_logic_arith.all;

use ieee.std_logic_unsigned.all;

entity advance_door_mealy is
    port
    (
        CLK: in std_logic; -- Clk
        RSET: in std_logic;-- Reset signal
        KEY: in std_logic_vector(3 downto 0); -- input keys
        LEDG: out std_logic_vector(2 downto 0);-- outputs
        LEDR :out std_logic---- output
    );
end advance_door_mealy;

architecture model of advance_door_mealy is
    type STATE_TYPE is (error, oppen, close,lock);
    signal state: STATE_TYPE;
    --variable TMP : std_logic;
begin
    clk_reset: PROCESS (rset,clk)
    BEGIN
        IF (rset='0') THEN
            state<= oppen;
        ELSIF rising_edge(clk) THEN
            case state is
```

```

when oppen =>
    if(KEY = "0001") then
        state<= close;

            LEDG<="010";
            LEDR <='0';
        elsif(KEY = "1000") then
            state<= error;

                LEDG<="000";
                LEDR <='1';

        else
            state <= oppen;

                LEDG<="001";
                LEDR <='0';

        end if;

        when close =>
            if(KEY = "0100") then
                state<=lock;

                    LEDG<="100";
                    LEDR <='0';

                elsif(KEY = "0010") then
                    state<= oppen;

                        LEDG<="001";
                        LEDR <='0';

                else
                    state <= close;

                        LEDG<="010";

```

```

        LEDR <='0';
    end if;

    when lock =>
        if(KEY = "0001") then
            state<= close;

            LEDG<="010";
            LEDR <='0';

            elsif(KEY = "1000") then
                state<= error;

                LEDG<="000";
                LEDR <='1';

            else
                state <= lock;

                LEDG<="100";
                LEDR <='0';

            end if;

            when error =>
                LEDG<="000";
                LEDR<='1';

                when others =>
                    LEDG<="111";

            end case ;

        end if;
    end process;
end model;

```

Advance door mealy do file

```
onerror {resume}

quietly WaveActivateNextPane {} 0

add wave -noupdate /advance_door_mealy_vhd_tst/CLK
add wave -noupdate /advance_door_mealy_vhd_tst/KEY
add wave -noupdate /advance_door_mealy_vhd_tst/LEDG
add wave -noupdate /advance_door_mealy_vhd_tst/LEDR
add wave -noupdate /advance_door_mealy_vhd_tst/RSET

TreeUpdate [SetDefaultTree]

WaveRestoreCursors {{Cursor 1} {0 ps} 0}

quietly wave cursor active 0

configure wave -namecolwidth 246
configure wave -valuecolwidth 100
configure wave -justifyvalue left
configure wave -signalnamewidth 0
configure wave -snapdistance 10
configure wave -datasetprefix 0
configure wave -rowmargin 4
configure wave -childrowmargin 2
configure wave -gridoffset 0
configure wave -gridperiod 1
configure wave -griddelta 40
configure wave -timeline 0
configure wave -timelineunits ps

update

WaveRestoreZoom {0 ps} {910 ps}
```

Advance door Test bench

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY advance_door_mealy_vhd_tst IS
```

```
END advance_door_mealy_vhd_tst;
```

```
ARCHITECTURE advance_door_mealy_arch OF advance_door_mealy_vhd_tst IS
```

```
-- constants
```

```
-- signals
```

```
SIGNAL CLK : STD_LOGIC;
```

```
SIGNAL KEY : STD_LOGIC_VECTOR(3 DOWNTO 0);
```

```
SIGNAL LEDG : STD_LOGIC_VECTOR(2 DOWNTO 0);
```

```
SIGNAL LEDR : STD_LOGIC;
```

```
SIGNAL RSET : STD_LOGIC;
```

```
COMPONENT advance_door_mealy
```

```
    PORT (
```

```
        CLK : IN STD_LOGIC;
```

```
        KEY : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
```

```
        LEDG : OUT STD_LOGIC_VECTOR(2 DOWNTO 0);
```

```
        LEDR : OUT STD_LOGIC;
```

```
        RSET : IN STD_LOGIC
```

```
    );
```

```
END COMPONENT;
```

```
BEGIN
```

```
    i1 : advance_door_mealy
```

```
    PORT MAP (
```

-- list connections between master ports and signals

CLK => CLK,

KEY => KEY,

LEDG => LEDG,

LEDR => LEDR,

RSET => RSET

);

clk_signal: process

begin

-----cLOCK SIGNAL-----

clk<='1';

wait for 10 ps;

--wait on clk, reset;

clk<='0';

wait for 10 ps;

--wait on clk, reset;

end process;

init : PROCESS

-- variable declarations

BEGIN

-- code that executes only once

-----CASE 1-----

KEY<= "1111"; --

rset<='1';

wait for 50ps ;

rset<='0';


```

        wait for 50ps ;

        rset<='1';

        wait for 50ps ;

KEY<= "0001"; -- close door

        wait for 50ps ;

        -----CASE 1-----

        KEY<= "0100"; -- lock door

        wait for 50ps ;

        -----

        KEY<= "0010"; -- open door

        wait for 50ps ;

        -----

        KEY<= "1000"; -- error

        wait for 50ps ;

        -----

        KEY<= "1111"; -- error

        wait for 50ps ;

        -----

        rset<='0';

        wait for 50ps ;

        rset<='1';

WAIT;

END PROCESS init;

always : PROCESS

-- optional sensitivity list

-- (      )

```

```
-- variable declarations

BEGIN

    -- code executes for every event on sensitivity list

WAIT;

END PROCESS always;

END advance_door_mealy_arch;
```